
29.-

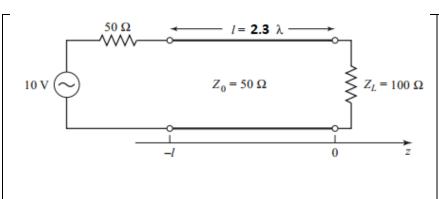

$$\Gamma(\ell) = \Gamma e^{-2j\beta\ell} e^{-2\alpha\ell} = \Gamma e^{-2\gamma\ell}$$

$$P_{\rm in} = \frac{|V_o^+|^2}{2Z_0} (1 - |\Gamma(\ell)|^2) e^{2\alpha\ell}$$

$$P_L = \frac{|V_o^+|^2}{2Z_0} (1 - |\Gamma|^2)$$

$$P_{\text{loss}} = P_{\text{in}} - P_L = \frac{|V_o^+|^2}{2Z_0} [(e^{2\alpha\ell} - 1) + |\Gamma|^2 (1 - e^{-2\alpha\ell})]$$



pozar_0_exercise_02_29.m



Z0=50 % ohm **Zgen=50**

Vgen=10 % Volt ZL=100

.....

syms lambda alpha_dB=.5/lambda % [dB/lambda] Np2dB=10*log10(exp(1)^2)

 $alpha_Np = alpha_dB/Np2dB$

beta=2*pi/lambda %[m^-1]

L=2.3*lambda % length of transmission line [m]

gamma=alpha_Np+1j*beta gamma_L=gamma*L

gamma_L_rad=double(gamma_L) % = 0.1323 +14.4513i

sometimes for the complex propagation constant gamma, units Np/m and degree are mixed as the solutions manual does. For this exercise the solutions manual shows $gamma=.1325+1j*108^{\circ}$. 108 degree is the remainder of $imag(gamma_degree)/360$

14.4513*180/pi-floor(14.4513*180/pi/360)*360

reflection coefficients on both sides of the transmission line refl_Load=(ZL-Z0)/(ZL+Z0)
refl_gen=refl_Load*exp(-2*gamma_L_rad)

TL input impedance (from generator)

 $\label{eq:continuous} \begin{subarray}{ll} Zin=Z0*(ZL+Z0*tanh(gamma_L_rad))/(Z0+ZL*tanh(gamma_$

 $alpha_dB = 1/(2*lambda)$

Np2dB = 8.685889638065037

alpha_Np =281474976710656/(4889721167171369*lambda)

 $gamma_L_rad = 0.132398642847158 + 14.451326206513048i$

= 1.079984984774065e+02

refl_Load = 0.3333333333333333

refl_gen = -0.206936161907528 + 0.150347922208021i

Zin = 31.588363022059227 + 10.163454575205781i

TL input power

Pin=(abs(Vgen*Zin/(Zgen+Zin)))^2/(2*Z0*(1-(abs(refl_gen))^2)*exp(2*real(gamma_L_rad))

 $P_{\text{in}} = \frac{1}{2} \text{Re} \{ V(-\ell) I^*(-\ell) \} = \frac{|V_o^+|^2}{2Z_0} (e^{2\alpha\ell} - |\Gamma|^2 e^{-2\alpha\ell})$ $= \frac{|V_o^+|^2}{2Z_0} (1 - |\Gamma(\ell)|^2) e^{2\alpha\ell}$

PLoad power reaching load

PLoad=(abs(Vgen*Zin/(Zgen+Zin)))^2/(2*Z0)*(1-(abs(refl_Load))^2)

lost power

Ploss=Pin-PLoad

Pin = 0.198382847405214

PLoad = 0.144789944222718

Ploss = 0.053592903182496

John Bofarull Guix jgb2012@sky.com attached: -- 1/4

PO ZAR chapter 02: exercise 29 ______ 04/06/2018 01:52:40.

Comment 1: perhaps of use too: maximum available power from generator

Pmax_gen=.5*(abs(Vgen))^2/(4*real(Zgen))

Pmax = 0.25

Alternatively

$$P(z) = P_0 e^{-2\alpha z} \quad \alpha = \frac{P_{\ell}(z=0)}{2P_0}$$

alpha_dB and alpha_Np are per metre.

alpha=double(alpha_Np*L)

Pout=Pin*exp(-2*alpha)

alpha = 0.132398642847158

Pout = 0.152231357248704

The solutions manual assumes

that would be all matched; generator to TL and TL to load.

absV0plus_all_match=abs(Vgen/2*exp(-real(gamma_L_rad)))

Instead from

$$V(z) = V_o^+ \left(e^{-\gamma z} + \Gamma e^{\gamma z} \right)$$

$$Z_{\text{in}} = \frac{V(-\ell)}{I(-\ell)} = Z_0 \frac{Z_L + Z_0 \tanh \gamma \ell}{Z_0 + Z_L \tanh \gamma \ell}.$$

$$V_o^+ = V_g \frac{Z_{\text{in}}}{Z_{\text{in}} + Z_g} \frac{1}{\left(e^{\gamma \ell} + \Gamma_{\ell} e^{-\gamma \ell}\right)}$$

$$V_o^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-\gamma \ell}}{(1 - \Gamma_\ell \Gamma_g e^{-2\gamma \ell})}$$

It's reasonable to consider that V0plus = $Vgen*Zin/(Zgen+Zin)*(exp(g_L)+refl_gen*exp(-gamma_L_rad))$ should be used, 2.89a in [POZAR] pg81

Vin=Vgen*Zin/(Zin+Zgen)*1/(exp(gamma_L_rad)+refl_gen*exp(-gamma_L_rad))
absVin=abs(Vin)

would be the correct start voltage for the procedure followed in the solutions manual. But because 2.92/93/94 are readily available, the answers have already been provided. This Pin is the same as the above used

 $Pin = (abs(Vgen*Zin)/(2gen+Zin)))^2/(2*Z0*(1-(abs(refl_gen))^2)*exp(2*real(gamma_L_rad))*(2*Zinder) + (2*Zinder)(2$

And it's not the other apparently correct

Vgen*Zin/(Zin+Zgen)

abs(Vgen*Zin/(Zin+Zgen))

Loss_dB=double(alpha_dB*L)
10*log10(Pin)-10*log10(PLoad)

10*log10(exp(2*alpha))

0.21 dB missing, the perturbation method is not exact

Generator and TL are matched, but TL and load are not. And it's not the other apparently correct **Vgen*Zin/(Zin+Zgen)**

abs(Vgen*Zin/(Zin+Zgen))

Comment: Zin with lossless TL would be

 $\label{eq:lossless} \textbf{Zin_lossless} = \textbf{Z0*(ZL+1j*Z0*tan(imag(gamma_L_rad)))}/(\textbf{Z0+1j*ZL*tan(imag(gamma_L_rad))})/(\textbf{Z0+1j*ZL*tan(imag(gamma_L_rad))})/(\textbf{Z0$

same as

 $Zin_lossless = Z0*(ZL+1j*Z0*tan(2*pi*2.3))/(Z0+1j*ZL*tan(2*pi*2.3))$

absV 0plus all match = 4.379958588165586

V in =

0.155584072758048 - 3.279133570422918i absV in = 3.282822471040817

= 3.965319190462363 + 0.751739611040107i

= 4.035947066681602

= 1.367657186248119 dB

= 1.1500000000000000

3.965319190462363 + 0.751739611040107i

26.928588541323347 +11.871170407231441i


Zin_lossless = 26.928588541323329 +11.871170407231373i

John Bofarull Guix jgb2012@sky.com attached: -- 2 / 4


PO ZAR chapter 02: exercise 29 ______ 04/06/2018 01:52:40.

```
Now with Smith Chart:
Z0=50; ZL=100;
sm1=smithchart; ax=gca; hold all;
refl_ZL=(ZL-Z0)/(ZL+Z0);
plot(ax,real(refl_ZL),imag(refl_ZL),...
                          'o','Color',[100],...
                          'LineWidth',2,...
                          'MarkerEdgeColor','b',...
                          'MarkerFaceColor',[.8.2.2],...
                          'MarkerSize',7)
                                                            % ZL
plot(ax,refl_mod(end).*cos(a(end)),refl_mod(end).*sin(a(end)),...
                          'o','Color',[100],...
                          'LineWidth',2,...
                          'MarkerEdgeColor','b',...
                          'MarkerFaceColor',[.2.8.2],...
                          'MarkerSize',7)
                                             % Zin at generator
[x_swr,y_swr]=Smith_plotGammaCircle(ax,ZL,Z0,[1.4.4])
refl_mod(end).*cos(a(end))+1j*refl_mod(end).*sin(a(end))
Zin_gen=Z0*(1+refl_in)/(1-refl_in)
[x_swr,y_swr]=Smith_plotGammaCircle(ax,Zin_gen,Z0,[.41.4])
SWR_Load=(1+abs(refl_ZL))/(1-abs(refl_ZL))
SWR_gen=(1+abs(refl_in))/(1-abs(refl_in))
str_swr_load=['SWR Load = 'num2str(SWR_Load)]
str_swr_gen=['SWR Generator = 'num2str(SWR_gen)]
legend(ax,'ZL','Zgen',str_swr_load,str_swr_gen)
```

legend(ax,'off')

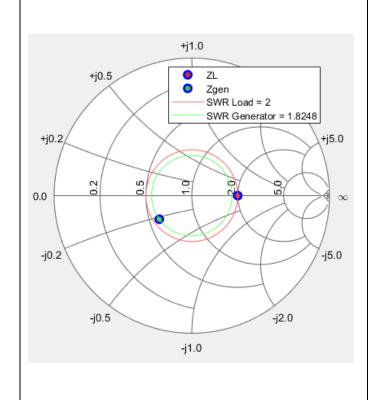


```
Smith plotRefLine2PhaseCircle(ax,ZL,Z0,[.61.6])
Smith_plotRefLine2PhaseCircle(ax,Zin_gen,Z0,[.61.6])
syms lambda
alpha_dB=.5/lambda % [dB/lambda]
Np2dB=10*log10(exp(1)^2);alpha_Np=alpha_dB/Np2dB
beta=2*pi/lambda;L=2.3*lambda
g=alpha_Np+1j*beta % g=gamma=alpha+1j*beta
g_L=g*L;g_L=double(simplify(g_L))
angle to run along TL: beta*L=pi rad means 360° around Smith Chart
so to match the imag(g_L) angle with Smith chart angle, double it.
N1=100
da=2*pi/N1 % angle differential for 2*pi around Smith Chart = lambda/2
amount_full_turns=floor(14.4513*180/pi/360)
angle rads left when no full turns left
14.4513-floor(14.4513*180/pi/360)
amount_da_rem=floor((14.4513-floor(14.4513*180/pi/360))/da)
total amount angle steps needed to achieve N1 resolution
N2=N1*amount full turns+amount da rem
a0=angle(refl_ZL)
a=double(linspace(a0,2*imag(g_L),N2));
refl_mod=linspace(refl_ZL,refl_ZL*exp(-real(g_L)),N2)
plot(ax,refl_mod.*cos(a),refl_mod.*sin(a),...
                           '-','LineWidth',.5,'Color',[1 0 0])
plot(ax,refl_mod(end).*cos(a(end)),refl_mod(end).*sin(a(end)),...
                                         'o','Color',[0 1 0],...
                                         'LineWidth',2,...
                                         'MarkerEdgeColor','b',...
                                'MarkerFaceColor',[.8.2.2],...
                                         'MarkerSize',7) % ZL
axis([-0.4008 0.3832 -0.4103 0.3737]
```

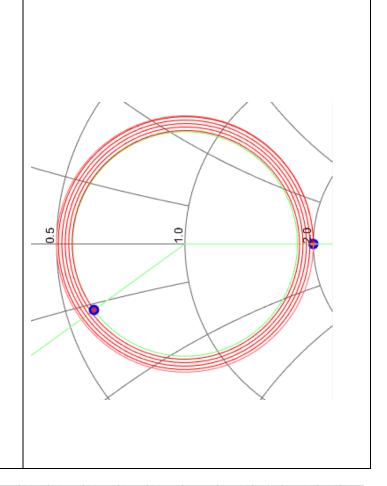


John Bofarull Guix jgb2012@sky.com attached: -- attached: --

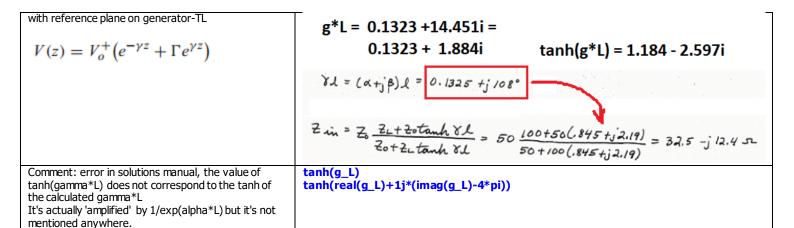PO ZAR chapter 02: exercise 29 ______ 04/06/2018 01:52:40.



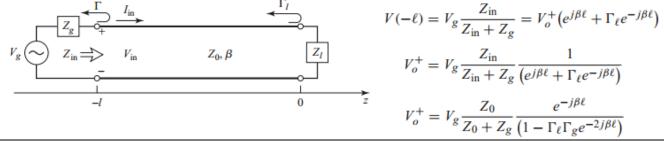the following expressions are for lossless transmission line



cannot be applied to lossy transmission lines because different input voltages are obtained:

 $\label{local-state-equation} $$ Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad))/(1-refl_Load*refl_gen*exp(-1j*2*imag(gamma_L_rad))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)))(1-refl_Load*refl_gen*exp(-1j*2*imag(gamma_L_rad)))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad))) $$ abs(Vgen*ZO/(ZO+Zgen)*exp(-1j*imag(gamma_L_rad)) $$ a$

John Bofarull Guix jgb2012@sky.com attached: -- 4/4